

# Logic Design (Part 3)

## Combinational Logic Devices (Chapter 3 + Notes)

Based on slides © McGraw-Hill  
Additional material © 2013 Farmer  
Additional material © 2020 Narahari

1

### Digital Logic Circuits

- we can build the basic logic gates using transistors
- Can build **any** boolean function using these gates
  - Theory underlying design of Boolean functions ..Boolean Algebra
    - Optimize circuit using Karnaugh maps
- **Power of abstraction....To build boolean functions, you can work with basic gates – no need to go down to the transistor level !!**
- Use these gates as building blocks to build more complex combinational circuits
  - Combinational Logic Devices: Adder, Multiplier, Multiplexer, Decoder, .....
  - ...any boolean function

2

## Definition: Combinational and Sequential Logic Circuits

- A circuit is a collection of devices that are physically connected by wires
  - Combinational circuit
  - Sequential circuit
- In Combinational circuit the input determines output
- In sequential circuit, the input and the previous 'state' (previous values) determine output and next 'state'
  - Need to 'remember' previous value – need **memory** device
  - Need circuit to implement concept of storage

3

## Recall our Goal....

- Design a machine that translates from natural language to electrons running around to solve the problem
  - We now have a device that controls how electrons run around
- Next: we want to build a computer
  - First step: Design a collection of logic devices that implement important functions that will be needed to build our computer
- S/W Analogy: When you write your software, you are using a collection of concepts, tools, IDEs and libraries
  - Each has been built, and tested, for you
  - All you have to do is combine them!

4

## Combinational Logic Devices

- We saw how we can build the simple logic gates using transistors and build **any** boolean function using these gates
- Use these gates as building blocks to build more complex combinational circuits
  - Decoder: based on value of n-bit input control signal, select one of  $2^N$  outputs
  - Multiplexer: based on value of N-bit input control signal, select one of  $2^N$  inputs.
  - Adder: add two binary numbers
  - ...any boolean function
- **SW Analogy: We are building a library of functions**
  - To design your solution, you can use any device in the library!

5

## Three Devices we focus on...

- N-bit Adder
  - Can build Subtract using Adder
- Decoder
  - Decode a bit string
- Multiplexer
  - A channel selector
- Other useful combinational logic devices
  - Multipliers
  - Shifters (but may need storage)
  - Comparators (to compare two numbers)
  - ...

6

## 1. N-bit Adder

- Add two N-bit numbers, represented in 2's complement
- Algorithm (for now): add corresponding bit positions, starting with least significant position, and propagate the carry bit leftward.
  - In practice: there are faster algorithms
  - Big-Oh Analysis:
    - To add N bit numbers how 'far' will the carry propagate ?

7

## Binary Addition

- Binary addition – just like base 10 (decimal) !
  - Add from right to left, propagating carry
  - Example using unsigned integers

$$\begin{array}{r}
 10010 \text{ (18)} \\
 + 01001 \text{ (9)} \\
 \hline
 11011 \text{ (27)}
 \end{array}
 \qquad
 \begin{array}{r}
 10010 \text{ (18)} \\
 + 01011 \text{ (11)} \\
 \hline
 11101 \text{ (29)}
 \end{array}
 \qquad
 \begin{array}{r}
 01111 \text{ (15)} \\
 + 00001 \text{ (1)} \\
 \hline
 10000 \text{ (16)}
 \end{array}$$

*carry* (curved arrow from bit 4 to bit 5 in the second example)  
*carry* (curved arrows from bit 3 to bit 4, bit 2 to bit 3, and bit 1 to bit 2 in the third example)

**Key Observation: We add one bit at a time**  
 therefore, building block is a 1-bit adder  
Use 1-bit adder to build N-bit adder!

8

## 1-bit Adder

- Two inputs A, B and Two outputs: S (sum) and Carry out (C)

- Truth table:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Problem?

- This works only for bit 0 where there is no Carry-in

- Called a half adder

- In general, we can have a carry-in input, so 3 inputs are A, B,  $C_{in}$  (carry-in) and 2 outputs S,  $C_{out}$  (carry out)

9

## Truth Table for Full-Adder

A	B	Carry In	Out	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

10


## Truth Table for Full-Adder

A	B	Carry In	Out	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

11
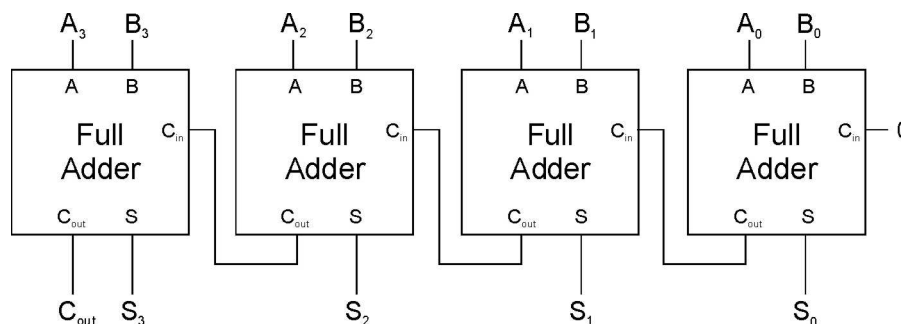
## N-bit Adder


- Use the building block of the full-adder to build N-bit adder
  - Need to connect carry-out to carry-in of next significant bit
- Example of 4-bit adder using 4 1-bit adders chained together (ripple carry adder)



12
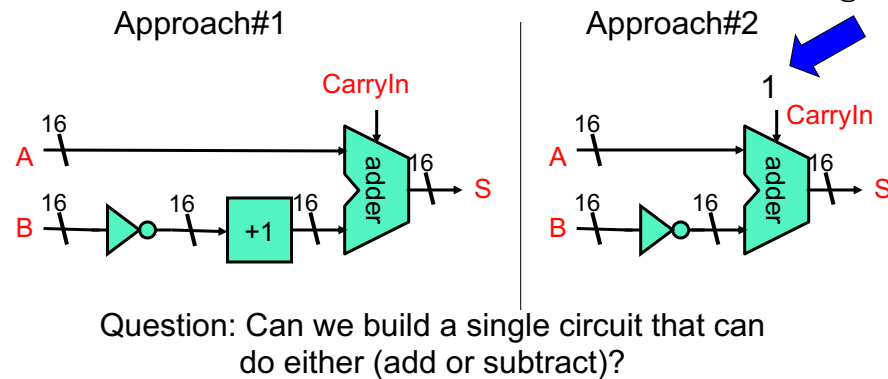
## How about a “subtractor?”

- Build a subtractor from out multi-bit adder
  - Calculate  $A - B = A + -B$
  - Negate B
  - Recall  $-B = \text{NOT}(B) + 1$



13

## The Decoder

- Useful for recognizing a particular bit pattern of 0's and 1's
- Connection to Computer Organization:
  - Program consists of instructions -- coded in binary (0's and 1's)
  - We want to look at a bit string for the instruction and determine what the instruction is
    - Is it an ADD or a MULT or a GOTO or.....
    - each instruction is given a unique encoding & decoder looks at the encoding and determines which ONE of the instructions the code corresponds to (i.e, which instruction has to be executed)
- In S/W, a “case”/switch statement:
  - One of the cases will be evaluated depending on value of 'input'

14


## Switch (case) statement in C

```
int x;
...
switch(x) {
    case 0: /* if x=0 call func Kevin */
        Kevin(); /* ex: Kevin does add */
        break;
    case 1: /* if x=1 call func Graham */
        Graham();
        break;
    case 2: /* if x=2 call func Sarah */
        Sarah(); /* ex: Sarah does AND */
        break;
    case 3: /* if x=3 call func Linnea */
        Linnea();
        break;
    default: printf("invalid value of x\n");
            break;
}
..
```

15
 
## N-2<sup>N</sup> Decoder

- N inputs – these represent the binary encoding of the 2<sup>N</sup> Outputs
  - Ex: if N=2, then 4 outputs 0,1,2,3, encoded to be 'switched on' when inputs are one of 00, 01, 10, 11 respectively
- Schematic:



16



## Designing a Decoder: Truth table 4 output lines $x_0, x_1, x_2, x_3$ & 2 inputs $a_1, a_0$

From truth table, design circuit:


$x_0 = a_1' \cdot a_0'$  (i.e., (NOT  $a_1$ ) AND (NOT  $a_0$ ))

$x_1 = a_1' \cdot a_0$        $x_2 = a_1 \cdot a_0'$        $x_3 = a_1 \cdot a_0$

$a_1$	$a_0$	$x_0$	$x_1$	$x_2$	$x_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

17

## Decoder

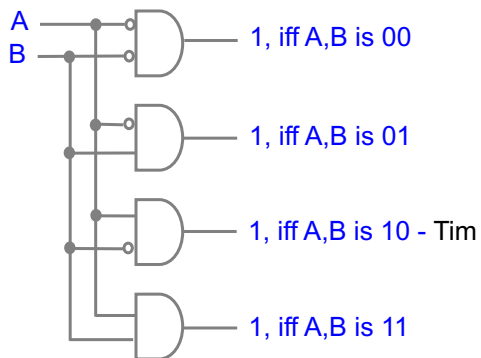


**2-bit decoder  
(4 input decoder)**

- An  $n$  input decoder has  $2^n$  outputs.
- Output  $i$  is 1 iff the binary value of the  $n$ -bit input is  $i$ .
- At any time, exactly one output is 1, all others are 0.

18
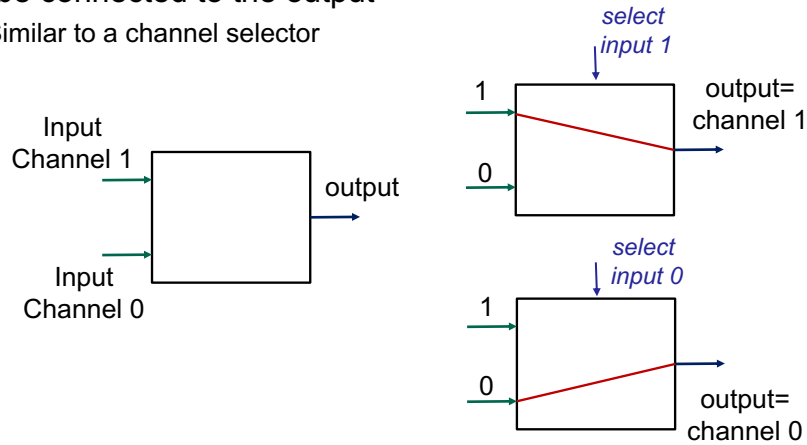
## The Multiplexer - selector

- Multiplexer (MUX) is a device that selects one of the inputs to be connected to the output
  - Similar to a channel selector




This is a 2-1 Multiplexer: Selects one of 2 inputs as the output


19
 
## N-1 Multiplexer

- Multiplexer selects one of the N inputs as the output
  - It needs  $\log_2 N$  'select lines' to determine which of the N inputs is selected to appear at the output
  - Schematic of a MUX:



 - Multi-bit muxes
  - Can switch an entire "bus" or group of signals
  - Switch n-bits with n muxes with the same select bits




20

## The Multiplexer (MUX) – 2-1 and 4-1 MUX

- Selector/Chooser of signals – *Imagine Switching Railroad Tracks*


- Multi-way switch

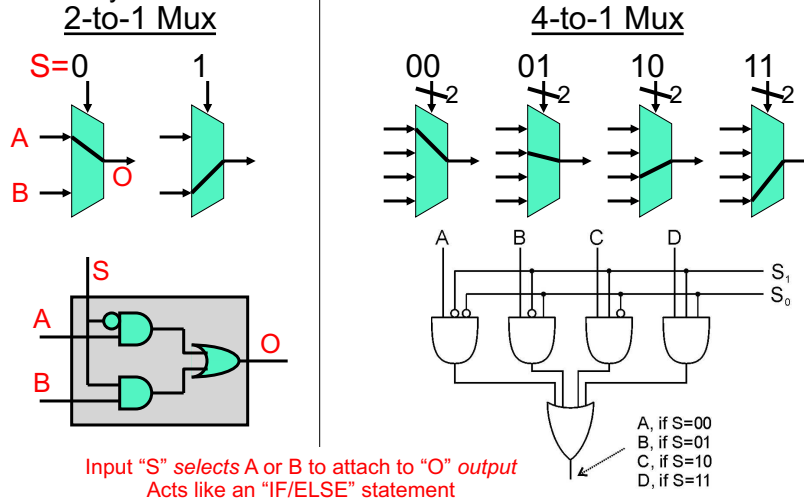

21


## Designing 4-1 MUX Using Logic Gates

### Multiplexer (MUX)

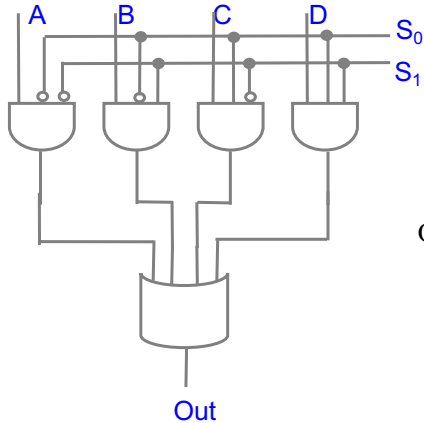

- In general, a MUX has
  - $2^n$  data inputs
  - n select (or control) lines
  - and 1 output.
- It behaves like a channel selector.
 
$$\text{Out} = A.\bar{S}_0.\bar{S}_1 + B.\bar{S}_0.S_1 + C.S_0.\bar{S}_1 + D.S_0.S_1$$




**A 4-to-1 MUX:**  
 Out takes the value of A, B, C or D  
 depending on the value of S (00, 01, 10, 11)  
 Out = A if S=00    Out = B if S = 01  
 Out = C if S=10    Out=D if S=11

22


## Designing 4-1 MUX Using Logic Gates

### Multiplexer (MUX)

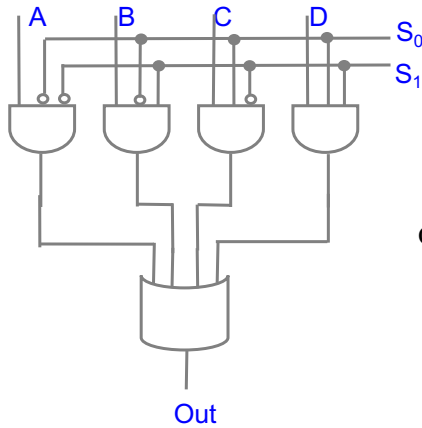

- In general, a MUX has
  - $2^n$  data inputs
  - $n$  select (or control) lines
  - and 1 output.
- It behaves like a channel selector.
 
$$\text{Out} = A.\bar{S}_0.\bar{S}_1 + B.\bar{S}_0.S_1 + C.S_0.\bar{S}_1 + D.S_0.S_1$$



#### A 4-to-1 MUX:

Out takes the value of A, B, C or D depending on the value of S (00, 01, 10, 11)


Out = A if S=00    Out = B if S = 01

Out = C if S=10    Out=D if S=11

23
 
### Example: MUX in a circuit

- Inputs A, B, C and x (select signal); Output F
- Devices/Gates: 2-1 MUX, AND gate



- If  $x=0$ , output of MUX = B and  $F = B.C$
- If  $x=1$ , output of MUX = A and  $F = A.C$
- Can write  $F = xAC + x'BC$

24

## Combinational vs. Sequential

### ▪ Combinational Circuit

- always gives the same output for a given set of inputs
  - ex: adder always generates sum and carry, regardless of previous inputs

### ▪ Sequential Circuit

- stores information
- output depends on stored information (state) plus input
  - so a given input might produce different outputs, depending on the stored information
- *example: vending machine*
  - Current total increases when you insert coins
  - output depends on previous state
- useful for building “memory” elements and “state machines”

25

## Next . . Circuits with “memory”

- First we need to build a device that can store a bit
  - Using our current ‘library’ of gates
  - Building memory follows
- How to model sequential circuits/machines
  - Methodology for designing these machines: Finite state machine
  - Model as a directed graph
- How to we “synchronize” and “coordinate” the different pieces in the circuit...enter the CLOCK
- can we use a sequential circuit to “control” how computations take place in a processor ?
- Is a sequential circuit = Computer ?
  - Limitations of sequential machines..more in Foundations course

26


## Appendix

27

## Binary Arithmetic: Half Adder

- Logical Function: **Half Adder**, implement Carry Out:

A	B	Sum	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Half Adder's Logic Function:



$$\text{SUM} = ((A' \text{ AND } B') \text{ OR } (A \text{ AND } B))'$$
$$\text{C} = ((A' \text{ AND } B') \text{ OR } (A' \text{ AND } B) \text{ OR } (A \text{ AND } B'))'$$

*Realize though: C = (A AND B), this isn't always best way!*



28
  
## Addition: Full Adders

- There is a limit with the half adder
  - It can't implement multiple-bit addition



  - It works for "least significant bit," but won't work for the next



- We need an adder that has 3 inputs and 2 outputs

3-29


29

## Truth Table

A	B	Carry In	Out	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

30


## Full Adder

 

31
 
## 1-bit Full Adder

▪ Add two bits and carry-in,  
produce one-bit sum and carry-out.





A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

32



## N-bit Adder

 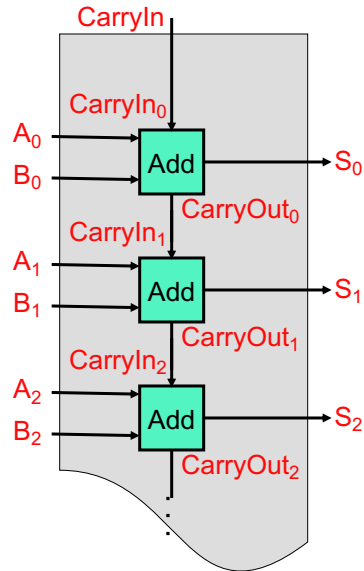


CarryOut: useful for detecting overflow

CarryIn: assumed to be zero if not present

3-33

33

## Four-bit Adder

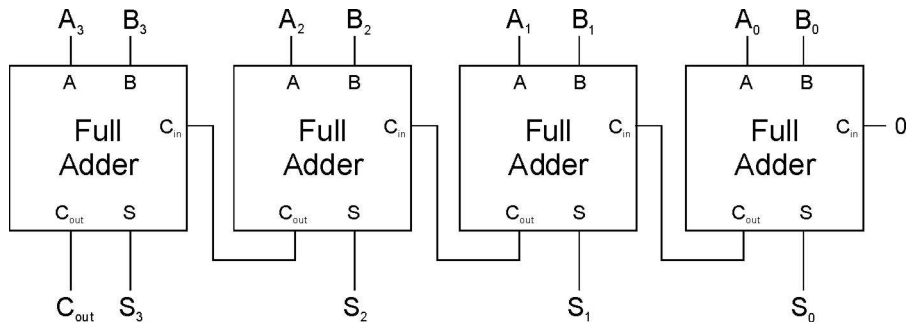


34

## A multi function Arithmetic Unit

- In a CPU, we'd like to do BOTH addition and subtraction
  - Can we give the CPU the ability to choose between two pieces of hardware?
  - Yes!
- Using a MUX to build a multifunction ALU


35
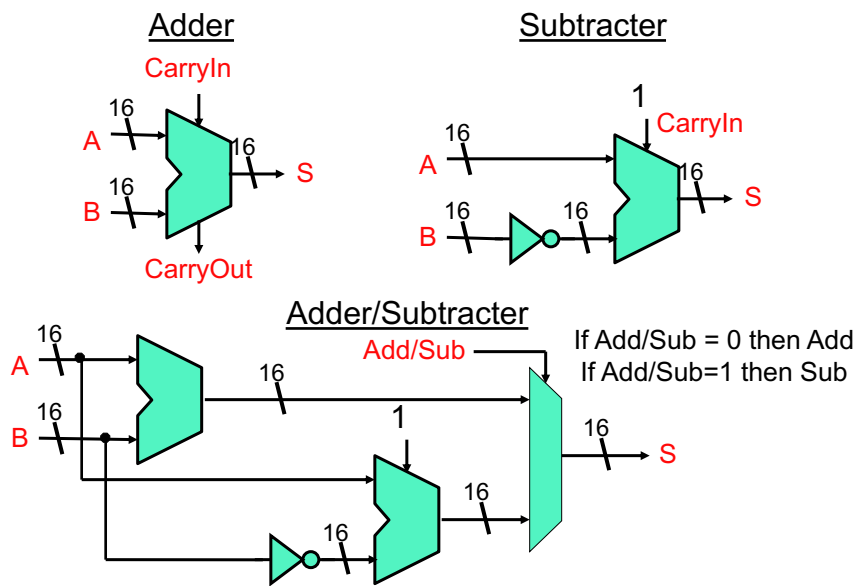
## Building an ALU using MUX Adder/Subtractor - Approach #1



36
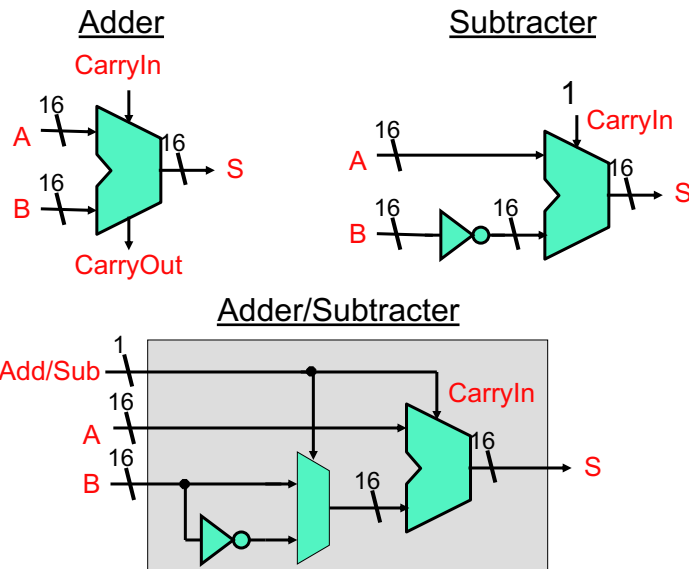
## Adder/Subtractor - Approach #2 (Optimize HW)



37

## Analysis of Circuits

- Download Example Circuits
  - In Cedar Logic: Set2.cdl
  - In Logisim: Set2.zip
    - Contains multiple files, titled Set2-Page1, Set2-Page2, etc.
    - Pages correspond to pages in the Set2.cdl file

38

## Analysis of circuits in file: Set2

- Page 1: Check truth table and identify behavior
- Page 2: Part of the circuit looks identical to Page1, but there is an additional 'output'.
  - Check truth table and identify behavior
- Page 3: This uses the circuit from Page2 and connects them (connects output of one circuit to input of next circuit).
  - Identify the function being implemented
- Page 4: If we treat 1-bit Adders as a Combinational logic device, then we can construct any N-bit adder using these devices
  - Bottom of the page has a schematic for a 4-bit adder
  - Input uses a Hex keyboard to input a 4-bit number
  - Uses a 7 segment LED display to display the 4-bit output as a hex number.
  - **Analogy with software design: Construct solution which utilizes functions**

39

## Analysis of circuits in file: Set2

- Page 5: Uses an adder, but adds some logic operations to the input X before it is sent to the Adder: Therefore adding Y and  $f(X)$  to get output Z
  - Inputs use Hex keyboards to send in 4-bit numbers
  - Determine what is  $f(x)$  and then determine what function is being implemented.
- Page 6: Examples of Multiplexer and Decoder
- Page 7: Circuit uses a multiplexer and gates
  - As you set the different select lines to the multiplexer, determine what the output is
  - Determine the behavior of the circuit and its 'function'
- Page 8: Circuit uses Multiplexer, Adder
  - Check truth table and identify behavior
- Page 9: Uses Decoder and Multiplexer
  - Determine values of select lines of multiplexer based on output of decoder
- Page 10: Example using a comparator

40